

priority encoder.

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY priority IS  
    PORT ( w : IN    STD_LOGIC_VECTOR(3 DOWNT0 0) ;  
          y : OUT STD_LOGIC_VECTOR(1 DOWNT0 0) ;  
          z : OUT STD_LOGIC ) ;  
END priority ;
```

```
ARCHITECTURE Behavior OF priority IS  
BEGIN
```

```
    WITH w SELECT  
        y <= "00" WHEN "0001",  
            "01" WHEN "0010",  
            "01" WHEN "0011",  
            "10" WHEN "0100",  
            "10" WHEN "0101",  
            "10" WHEN "0110",  
            "10" WHEN "0111",  
            "11" WHEN OTHERS ;
```

```
    WITH w SELECT  
        z <= '0' WHEN "0000",  
            '1' WHEN OTHERS ;
```

```
END Behavior ;
```



**Selected
Signal
Assignment**

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```


```
ENTITY priority IS
```

```
    PORT ( w  : IN    STD_LOGIC_VECTOR(3 DOWNT0 0) ;  
          y   : OUT  STD_LOGIC_VECTOR(1 DOWNT0 0) ;  
          z   : OUT  STD_LOGIC ) ;
```

```
END priority ;
```

```
ARCHITECTURE Behavior OF priority IS  
BEGIN
```

```
    y <= "11" WHEN w(3) = '1' ELSE  
        "10" WHEN w(2) = '1' ELSE  
        "01" WHEN w(1) = '1' ELSE  
        "00" ;  
    z <= '0' WHEN w = "0000" ELSE '1' ;  
END Behavior ;
```



**Conditional
Signal
Assignment**

Hierarchical code for a 16-to-1
multiplexer
using 4-to-1 mux

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
LIBRARY work ;
USE work.mux4to1_package.all ;

ENTITY mux16to1 IS
    PORT ( w   : IN    STD_LOGIC_VECTOR(0 TO 15) ;
          s   : IN    STD_LOGIC_VECTOR(3 DOWNT0 0) ;
          f   : OUT   STD_LOGIC ) ;
END mux16to1 ;

ARCHITECTURE Structure OF mux16to1 IS
    SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;
BEGIN
    Mux1: mux4to1 PORT MAP
        ( w(0), w(1), w(2), w(3), s(1 DOWNT0 0), m(0) ) ;
    Mux2: mux4to1 PORT MAP
        ( w(4), w(5), w(6), w(7), s(1 DOWNT0 0), m(1) ) ;
    Mux3: mux4to1 PORT MAP
        ( w(8), w(9), w(10), w(11), s(1 DOWNT0 0), m(2) ) ;
    Mux4: mux4to1 PORT MAP
        ( w(12), w(13), w(14), w(15), s(1 DOWNT0 0), m(3) ) ;
    Mux5: mux4to1 PORT MAP
        ( m(0), m(1), m(2), m(3), s(3 DOWNT0 2), f ) ;
END Structure ;

```

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
USE work.mux4to1_package.all ;
```

```
ENTITY mux16to1 IS  
    PORT ( w  : IN    STD_LOGIC_VECTOR(0 TO 15) ;  
          s  : IN    STD_LOGIC_VECTOR(3 DOWNT0 0) ;  
          f  : OUT STD_LOGIC ) ;  
END mux16to1 ;
```

```
ARCHITECTURE Structure OF mux16to1 IS  
    SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;  
BEGIN  
    G1: FOR i IN 0 TO 3 GENERATE  
        Muxes: mux4to1 PORT MAP (  
            w(4*i), w(4*i+1), w(4*i+2), w(4*i+3), s(1 DOWNT0 0), m(i) ) ;  
    END GENERATE ;  
    Mux5: mux4to1 PORT MAP ( m(0), m(1), m(2), m(3), s(3 DOWNT0 2), f ) ;  
END Structure ;
```

Hierarchical code for a 4-to-16
binary decoder.

```

Library ieee;
use ieee.std_logic_1164.all;
Library work;
use work.dec2to4_package.all;

```

```

entity dec4to16 is
    Port (
        w : in STD_LOGIC_VECTOR(3 downto 0);
        En : in STD_LOGIC;
        y : out STD_LOGIC_VECTOR(0 to 15)
    );

```

```

end dec4to16;

```

```

architecture structure of dec4to16 is
    signal m : STD_LOGIC_VECTOR(0 upto 3);

```

```

begin

```

```

    DEC1 : dec2to4 Port map (w(3), w(2), En, m);

```

```

    G1 : For i IN 0 to 3 Generate
        DEC2 : dec2to4 Port map

```

```

            ( w(1), w(0), m(i), y(4*i), y(4*i+1), y(4*i+2),
              y(4*i+3)
            );

```

```


    end Generate;

```

```

end architecture;

```
 
```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY shifter IS
    PORT ( w      : IN    STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          Shift   : IN    STD_LOGIC ;
          y       : OUT   STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          k       : OUT   STD_LOGIC ) ;
END shifter ;

ARCHITECTURE Behavior OF shifter IS
BEGIN
    PROCESS (Shift, w)
    BEGIN
        IF Shift = '1' THEN
            y(3) <= '0' ;
            y(2 DOWNTO 0) <= w(3 DOWNTO 1) ;
            k <= w(0) ;
        ELSE
            y <= w ;
            k <= '0' ;
        END IF ;
    END PROCESS ;
END Behavior ;

```


```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.numeric_std.all ;

ENTITY shifter IS
    PORT ( w      : IN    UNSIGNED(3 DOWNT0 0) ;
          Shift   : IN    STD_LOGIC ;
          y      : OUT   UNSIGNED(3 DOWNT0 0) ;
          k      : OUT   STD_LOGIC ) ;
END shifter ;

ARCHITECTURE Behavior OF shifter IS
BEGIN
    PROCESS (Shift, w)
    BEGIN
        IF Shift = "1" THEN
            y <= w SRL 1 ;
            k <= w(0) ;
        ELSE
            y <= w ;
            k <= "0" ;
        END IF ;
    END PROCESS ;
END Behavior ;

```

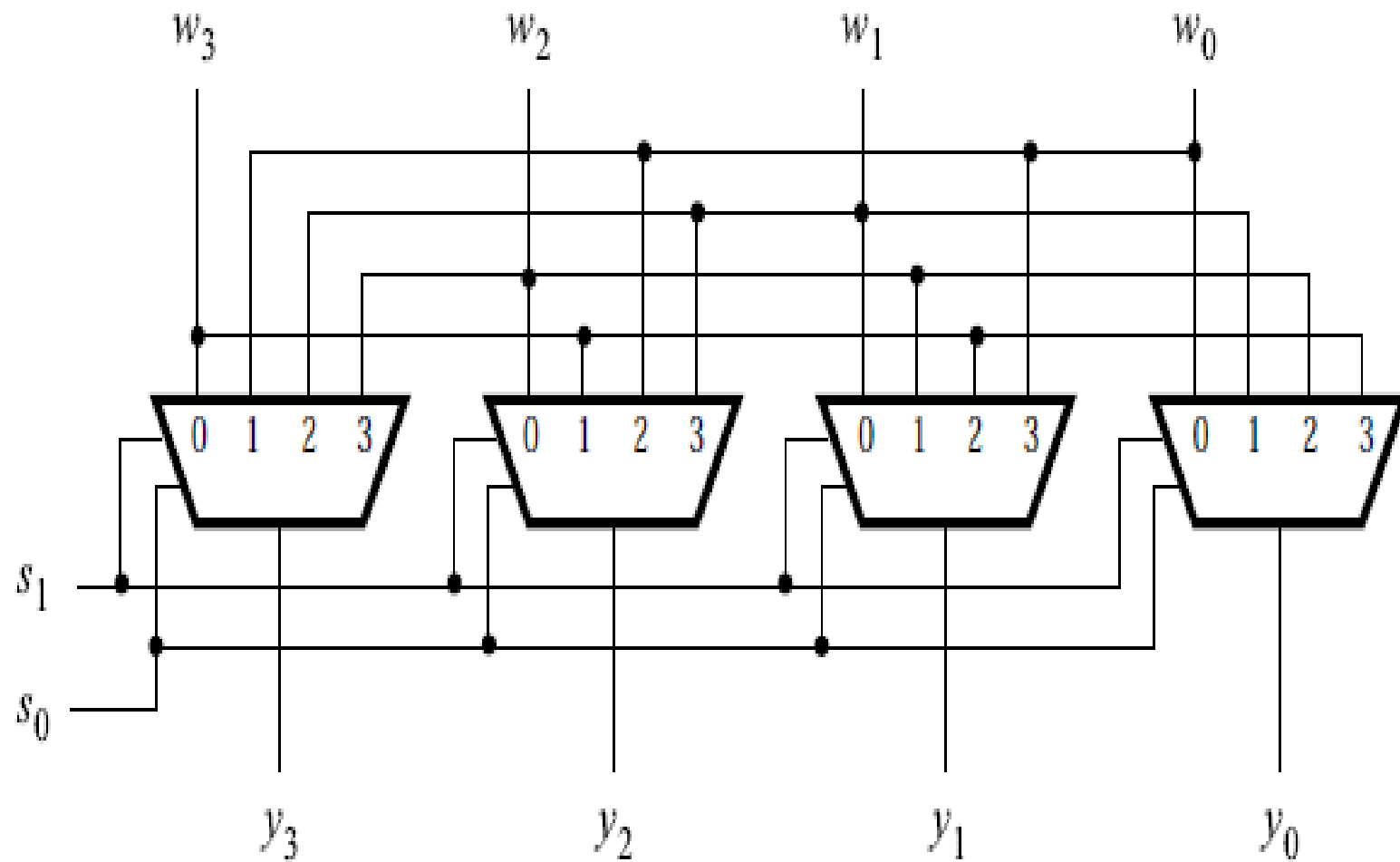

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.numeric_std.all ;

ENTITY barrel IS
    PORT ( w  : IN    UNSIGNED(3 DOWNT0 0) ;
          s  : IN    UNSIGNED(1 DOWNT0 0) ) ;
          y  : OUT   UNSIGNED(3 DOWNT0 0) ) ;
END barrel ;

ARCHITECTURE Behavior OF barrel IS
BEGIN
    PROCESS (s, w)
    BEGIN
        CASE s IS
            WHEN "00" =>
                y <= w ;
            WHEN "01" =>
                y <= w ROR 1 ;
            WHEN "10" =>
                y <= w ROR 2 ;
            WHEN OTHERS =>
                y <= w ROR 3 ;
        END CASE ;
    END PROCESS ;
END Behavior ;

```

Rom

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned;

```

```

entity ram is
  port (
    Addr : in std_logic_vector(2 downto 0);
    Dout : out std_logic_vector(15 downto 0);
  );
end ram;

```

architecture dataflow of ram is

```

  signal Temp : integer range 0 to 7;
  type ram_array is array (0 to 7) of std_logic_vector(15 downto 0);
  constant memory : ram_array :=

```

```

  (
    X"200A",
    X"0459",
    X"A412",
    X"0598",
    X"CD0F",
    X"F103",
    X"5312",
    X"0013"
  );

```

begin

```

  Temp <= to_integer(addr);

```

```


  Dout <= memory(Temp);

```

end dataflow;

RAM

read & write. RAM داتا سلاش

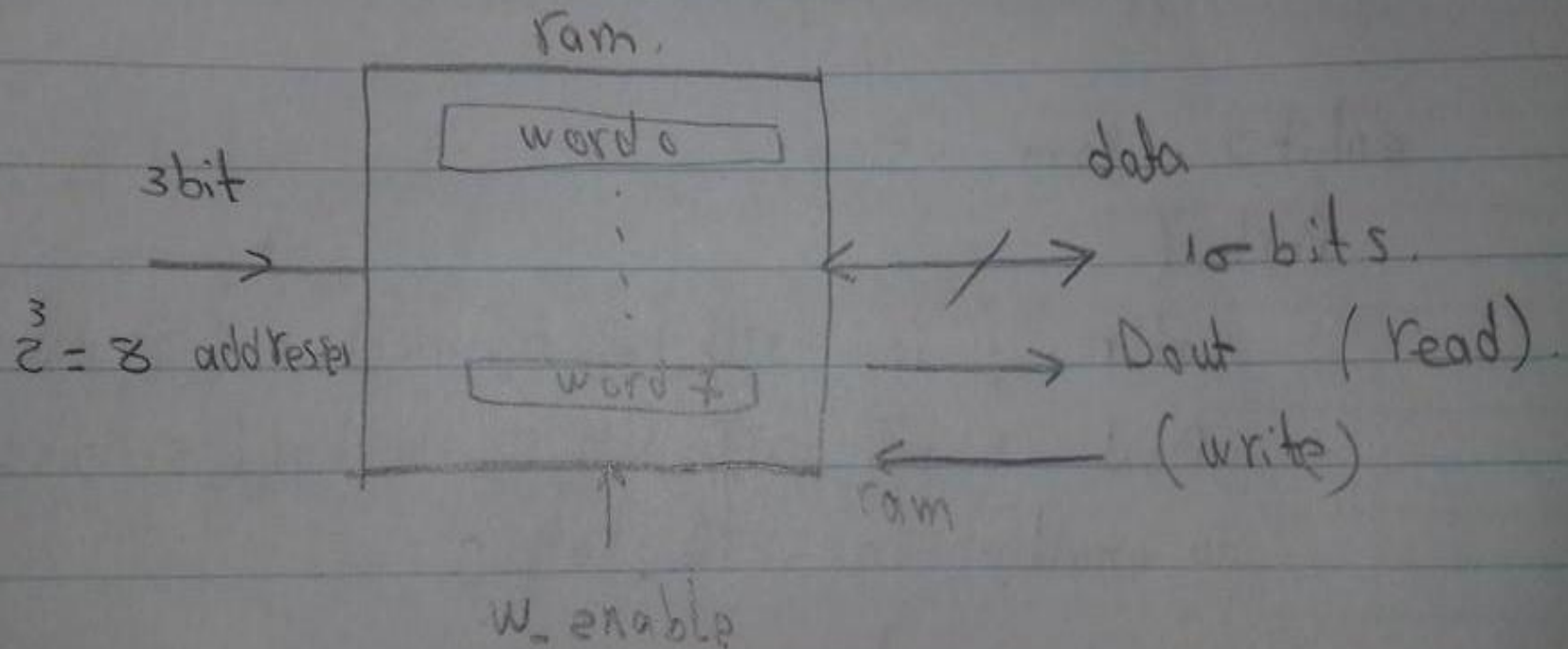

	0	5617
	1	AB03
	2	F032
	3	EB70
→	4	0134
addresses	5	D213
= integer(addr)	6	304A
= 2^3	7	BA30

```
library ieee;  
use ieee.STD_logic_1164.all;  
use ieee.STD_logic_unsigned;
```

```
entity ram is
```

```
  port (
```

```
    addr : in STD_logic_vector (7 downto 0);
```

```
    Dout : out STD_logic_vector (15 downto 0);
```

```
    w_enable : in STD_logic  
  );
```

```
end ram;
```

architecture dataflow of ram is

signal Temp : integer range 0 to 7;

type ram_array is array (0 to 7) of STD_logic_vector
 (15 downto 0);

constant memory : ram_array :=

```
(  
    x"5617",  
    x"AB03",  
    x"F032",  
    x"EB70",  
    x"0134",  
    x"D213",  
    x"304A",  
    x"BA30")
```

Begin

Process (addr , w_enable , Temp) .

begin

Temp <= to_integer (addr) .

if (w_enable = '0') then .

 Dout <= memory (Temp) ;

else


 memory (Temp) <= Dout ;

endif .

end Process

end data flow ;



 

```

Process (sets a, b, c, d)
begin.
if ( sel(2) = '1' ) then
    y <= A ;
else if ( sel(1) = '1' ) then
    y <= B ;
else if ( sel(0) = '1' ) then
    y <= C ;
else
    y <= D ;
end if ;
end Process ;
  
```

ex

architecture Var of EF is

signal temp: std_logic;

begin

process (clk, Temp, a, b)

begin

if reset = '1' then

out <= '0';


elseif (clk'event and clk = '1') then


temp <= a or b;

out <= temp;

end process;


end var;

 

 

Temp 11:00 AM 11/11/2020 D input out 11:11

ex

 

```

process ( clk, reset, set )
begin
    if ( reset = '1' ) then
        out <= '0';
    else if ( clk'event and clk = '1' ) then
        if ( set = '1' ) then
            out <= a and b;
        else
            out <= c and d;
        end if;
    end if;
end process;

```